

Green Light-Emitting Diode (LED) Transient Current Simulation

1 Introduction

This application note addresses the issue of determining the transient current in a DC series circuit that includes an LED, which is a non-linear electro-optical component. Without an LED in the circuit, a differential equation with its explicit analytical solution (by inspection) are shown below:

$$\dot{I} = -I/(RC) \text{ with } I(0) = V_S/R$$

and

$$I = V_S/R e^{(-t/(RC))}$$

However, with an LED in the circuit, a differential equation, for which there is no explicit analytical solution is developed in section 2. Analog computation to the rescue!

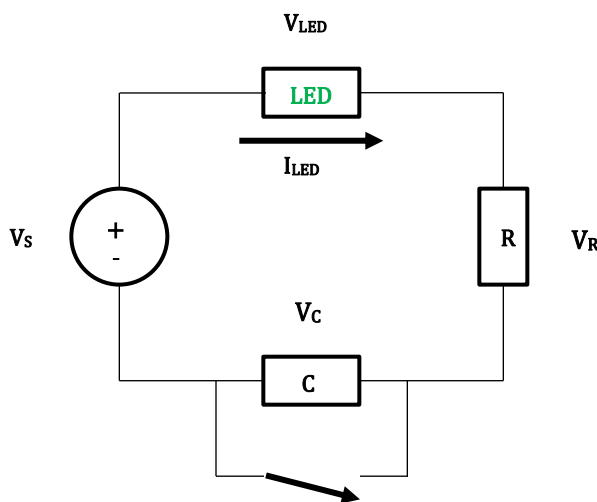


Figure 1: LED-resistor-capacitor series circuit

2 Mathematical modeling

Starting with the ideal light-emitting diode equation,

$$I_{LED} = I_{RS}[e^{(V_{LED}/(\eta kT/q))} - 1] \quad (1)$$

where

I_{RS} = diode reverse saturation current

η = ideality factor

k = the Boltzmann constant

T = LED junction temperature

q = electron charge magnitude

Letting $V^* = \eta kT/q$,

$$I_{LED} = I_{RS}[e^{(V_{LED}/V^*)} - 1]$$

Solving for V_{LED} ,

$$V_{LED} = V^*[\ln(I_{LED} + I_{RS}) - \ln(I_{RS})] \quad (2)$$

Differentiating (2) with respect to t ,

$$dV_{LED}/dt = V^*/(I_{LED} + I_{RS}) dI_{LED}/dt \quad (3)$$

According to DC circuit theory (see figure 1),

$$V_R + V_C + V_{LED} = V_S$$

$$RI_{LED} + Q/C + V^*[\ln(I_{LED} + I_{RS}) - \ln(I_{RS})] = V_S \quad (4)$$

Differentiating (4) with respect to t ,

$$RdI_{LED}/dt + 1/C dQ/dt + V^*/(I_{LED} + I_{RS})dI_{LED}/dt = 0 \text{ or}$$

$$R\dot{I}_{LED} + 1/C \dot{I}_{LED} + V^*/(I_{LED} + I_{RS}) \dot{I}_{LED} = 0$$

$$R\dot{I}_{LED} + 1/C \dot{I}_{LED} + V^*/(I_{LED} + I_{RS}) \dot{I}_{LED} = 0$$

$$(R + V^*/(I_{LED} + I_{RS})) \dot{I}_{LED} = -1/C I_{LED}$$

$$(1 + V^*/(R(I_{LED} + I_{RS}))) \dot{I}_{LED} = -1/(RC) I_{LED}$$

Letting $\tau = RC$,

$$(1 + V^*/(R(I_{LED} + I_{RS}))) \dot{I}_{LED} = -I_{LED}/\tau$$

$$\dot{I}_{LED} = -1/\tau \times I_{LED}/(1 + V^*/(R(I_{LED} + I_{RS})))$$

$$\dot{I}_{LED} = -1/\tau \times I_{LED}(I_{LED} + I_{RS})/(I_{LED} + I_{RS} + V^*/R) \text{ with } I_{LED}(0) = I_{LED0} \quad (5)$$

Letting

$$\tau = RC = 3.3 \text{ k}\Omega \times 470 \text{ }\mu\text{F} = 1.55 \text{ s},$$

$$I_{RS} = 0 \text{ mA},$$

$$I_{LED}(0) = 2.50 \text{ mA},$$

$$V^*/R = 0.050 \text{ mA}, \text{ and}$$

$I_{LED} = I$, then

$$\dot{I} = -I^2/(1.55 \text{ s}(I + 0.050 \text{ mA})) \text{ with } I(0) = 2.50 \text{ mA} \quad (6)$$

Suppressing units,

$$\dot{I} = -I^2/(1.55(I + 0.050)) \text{ with } I(0) = 2.50 \quad (7)$$

3 Computer setup

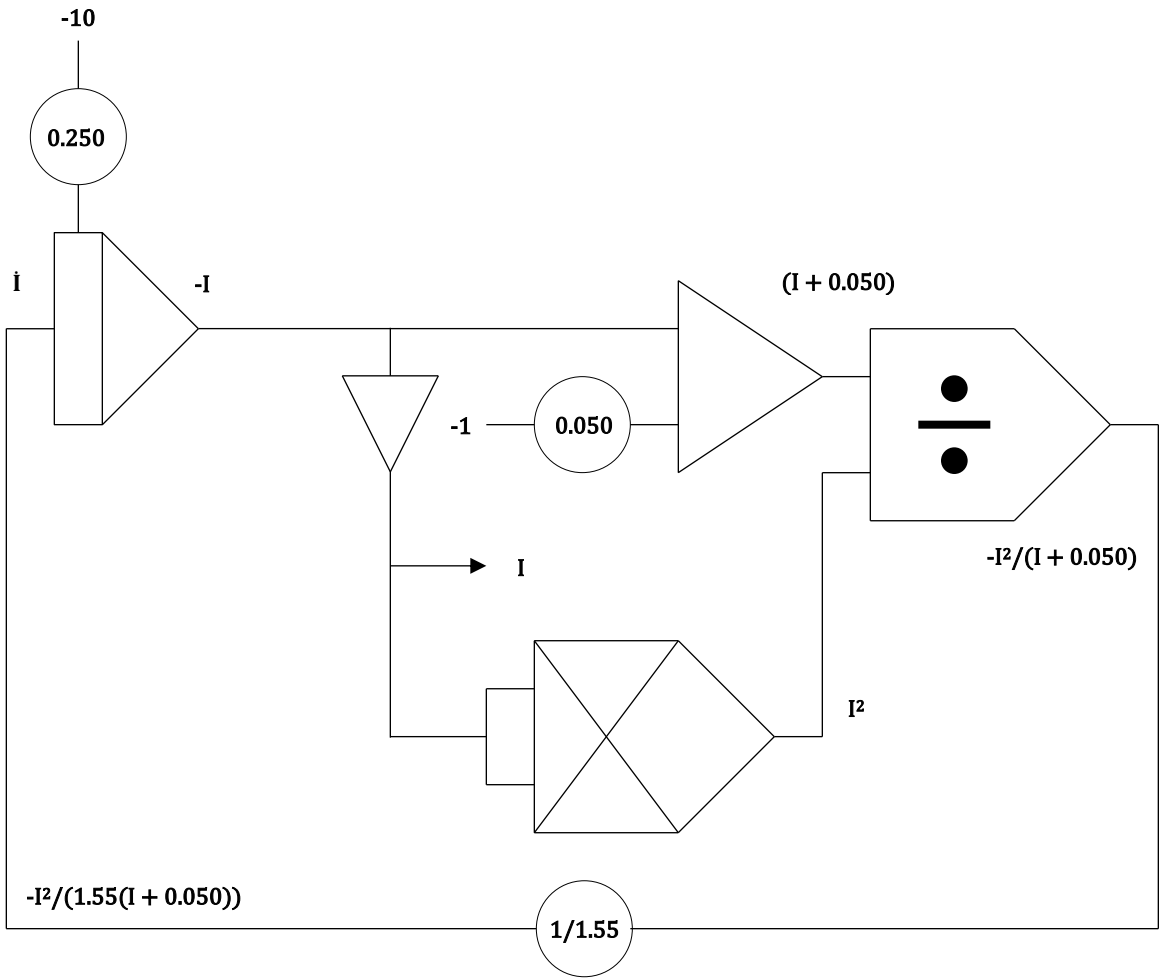


Figure 2: Computer setup for green LED transient current simulation

4 Results

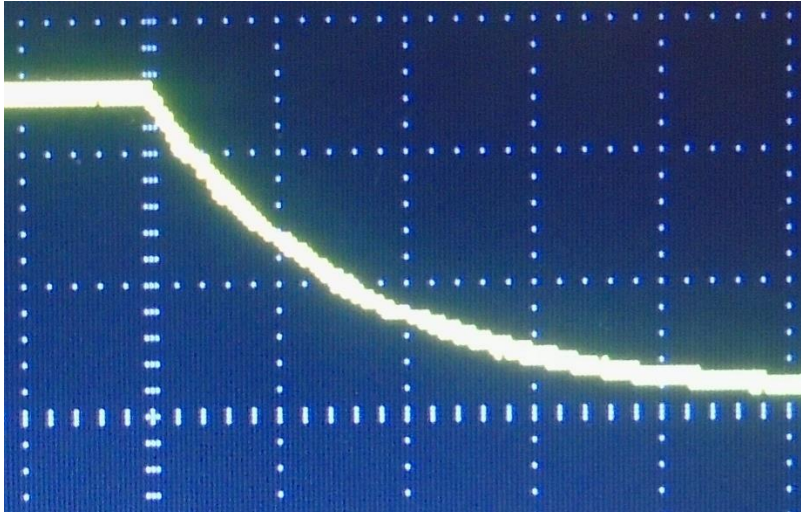


Figure 3: Green LED transient current vs time*

*For this application note, the display was produced during a single run by a differential equation analog computer prototype using discrete components with tolerances between 1% and 10%.

Michael Cimososi, Issue #4, 18-NOV-2020